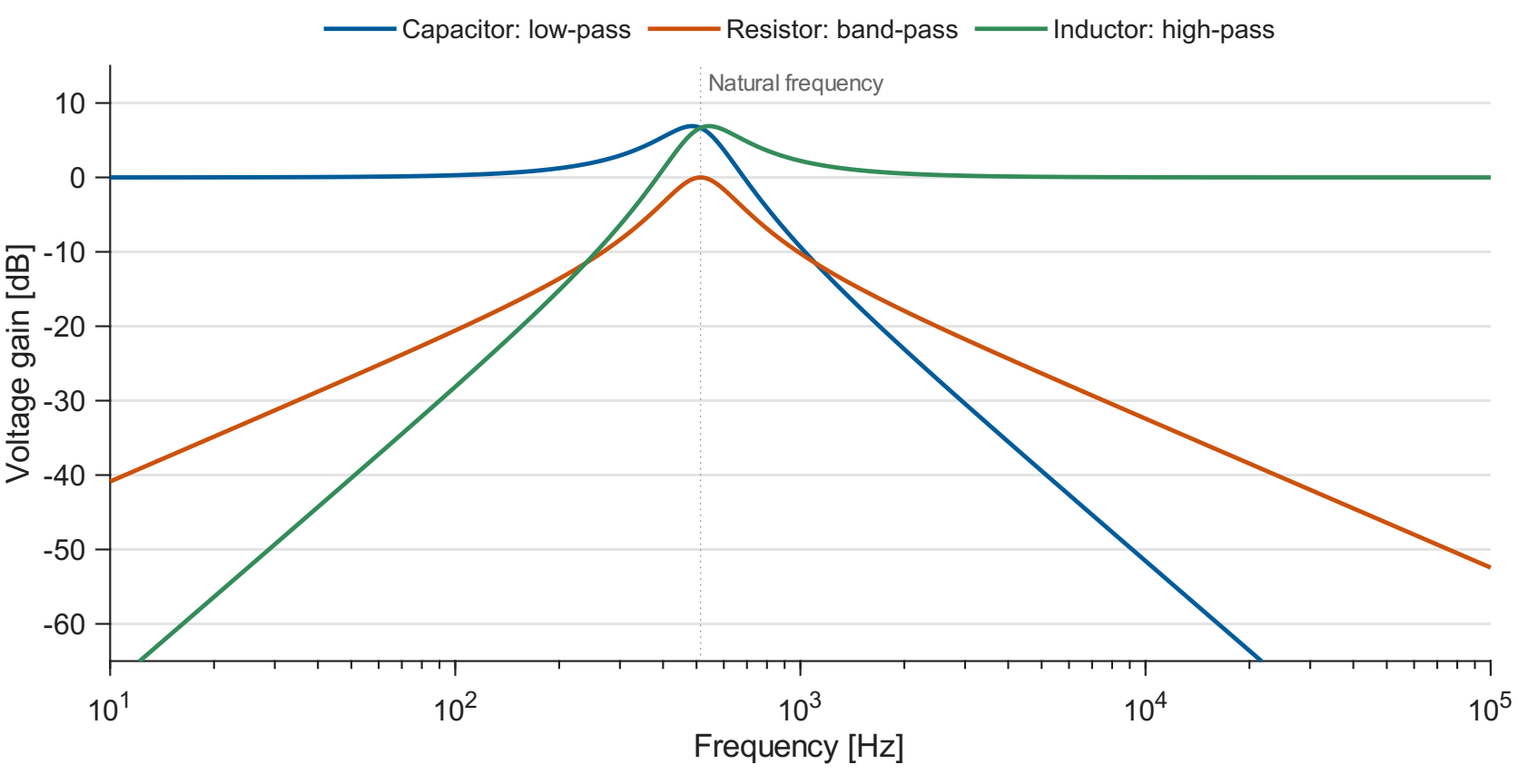
Capacitor: low-pass
Resistor: band-pass
Inductor: high-pass
Natural frequency
10
0
-10
-20
-30
-40
-50
-60
Voltage gain [dB]
10^1
10^2
10^3
10^4
10^5
Frequency [Hz]